

*Note: Late HW is **not** accepted! Put your "last name, first name," the course number (3701), and the HW number in the top right hand corner of the first page of all HW assignments. Also for all homework, use file name **HWx.pdf**. Do **NOT** put your social security number or your UF ID number on your HW.*

- Design by direct implementation the logic diagrams (by hand) for the following logic equations using **any** real 1-input, 2-input or 3-input logic gates, trying to minimize the total number of gates. You may choose **any** activation level for inputs and outputs that will simplify your design. (Do **not** simplify the equations.)
  - $V = A * [ / (B * /C) + C * D ]$
  - $W = A * B * /C + / (A * B * C)$
  - $U = / (A * B + /C)$

**Below are for practice only**, i.e., they do **not** need to be submitted.

- $Y = / (A * B) * C$
- $Z = (/A + /B) * /C$

- Now redesign the above with any real 1-input, 2-input or 3-input logic gates, again trying to minimize the total number of gates, but this time assume the inputs are active-high and the outputs are active-low. (Do **not** simplify.)
- Now redesign the above, but this time use **only** the following 1-input, 2-input or 3-input gates: AND (no bubbles) [which is also an OR with bubbles at inputs and output], OR (no bubbles) [which is also an AND with bubbles everywhere] and Level Shifter. Assume the inputs and outputs are **all active-high**. (Do **not** simplify.)
- Design by direct implementation the logic diagrams (by hand) for the following logic equations using any mixed-logic equivalent of 2-input NAND gates. (You may use an AND gate with no bubbles at its inputs and a bubble at the output or use an OR gate with bubbles on the inputs and no bubble on the output). You must create level-shifters (as needed) with a NAND gate. (Do **not** simplify the equations.)

a) $X = A * /B + A * C$	Active-high: A, B, C, X	Active-low: (none)
b) $X = A * /B + A * C$	Active-high: C	Active-low: A, B, X
c) $X = A * /B + A * C$	Active-high: (none)	Active-low: A, B, C, X
- In this problem, you will design **new** logic diagrams for problems 1 c and 4 c, optimizing the solution to use a minimum number of gates and chips. You may use whatever real chips you like in this problem. Assume that these two circuits make up a single design so that unused parts of one chip for the first circuit can be used for the second circuit. Use the following activation levels: B and C are active-high, A is active-low. Choose any desired activation level for the outputs. Show chip and pin numbers for both circuits. (Do **not** simplify.)