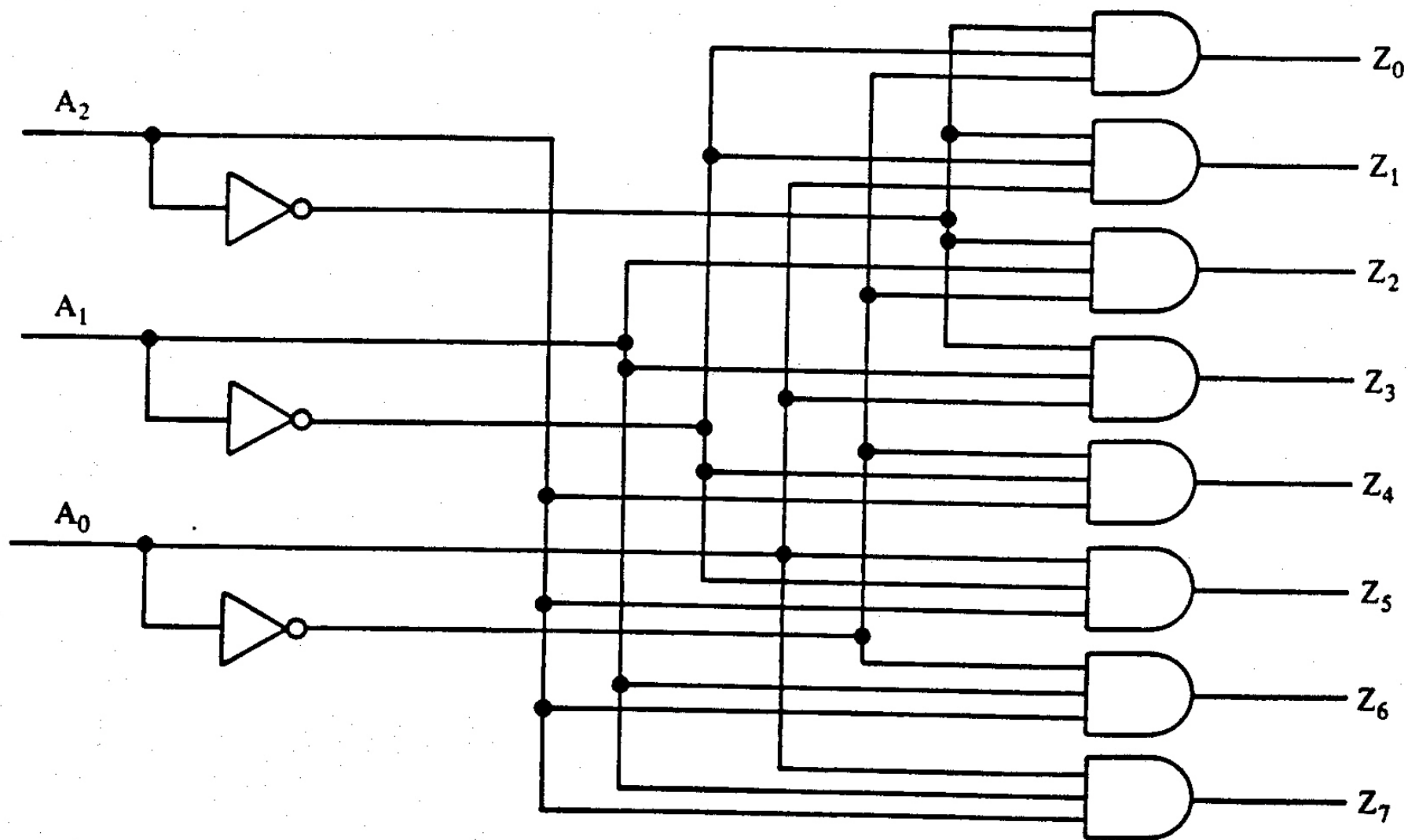


(a) Functional block diagram

A_2	A_1	A_0	Z_0	Z_1	Z_2	Z_3	Z_4	Z_5	Z_6	Z_7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

(b) Truth table

Figure 4.9 3-to-8 decoder.



(c) Design and realization

Figure 4.9 3-to-8 decoder.


 


Figure 9-14a:
A 4-to-10 Line
Decoder

(a) Logic diagram

Roth Textbook

 


(a) Functional block diagram


Figure 4.10 74'138 decoder.

Inputs						Outputs							
E ₁	E ₂	E ₃	A ₂	A ₁	A ₀	Z ₀	Z ₁	Z ₂	Z ₃	Z ₄	Z ₅	Z ₆	Z ₇
H	X	X	X	X	X	H	H	H	H	H	H	H	H
X	H	X	X	X	X	H	H	H	H	H	H	H	H
X	X	L	X	X	X	H	H	H	H	H	H	H	H
L	L	H	L	L	L	L	H	H	H	H	H	H	H
L	L	H	L	L	H	H	L	H	H	H	H	H	H
L	L	H	L	H	L	H	H	L	H	H	H	H	H
L	L	H	L	H	H	H	H	H	L	H	H	H	H
L	L	H	H	L	L	H	H	H	H	L	H	H	H
L	L	H	H	L	H	H	H	H	H	H	L	H	H
L	L	H	H	H	L	H	H	H	H	H	H	L	H
L	L	H	H	H	H	H	H	H	H	H	H	H	L

(b) Voltage table

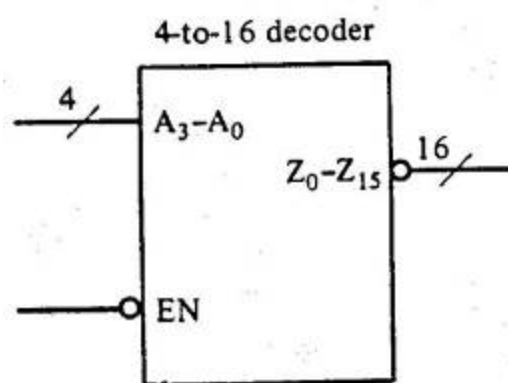


(c) Functional block diagram

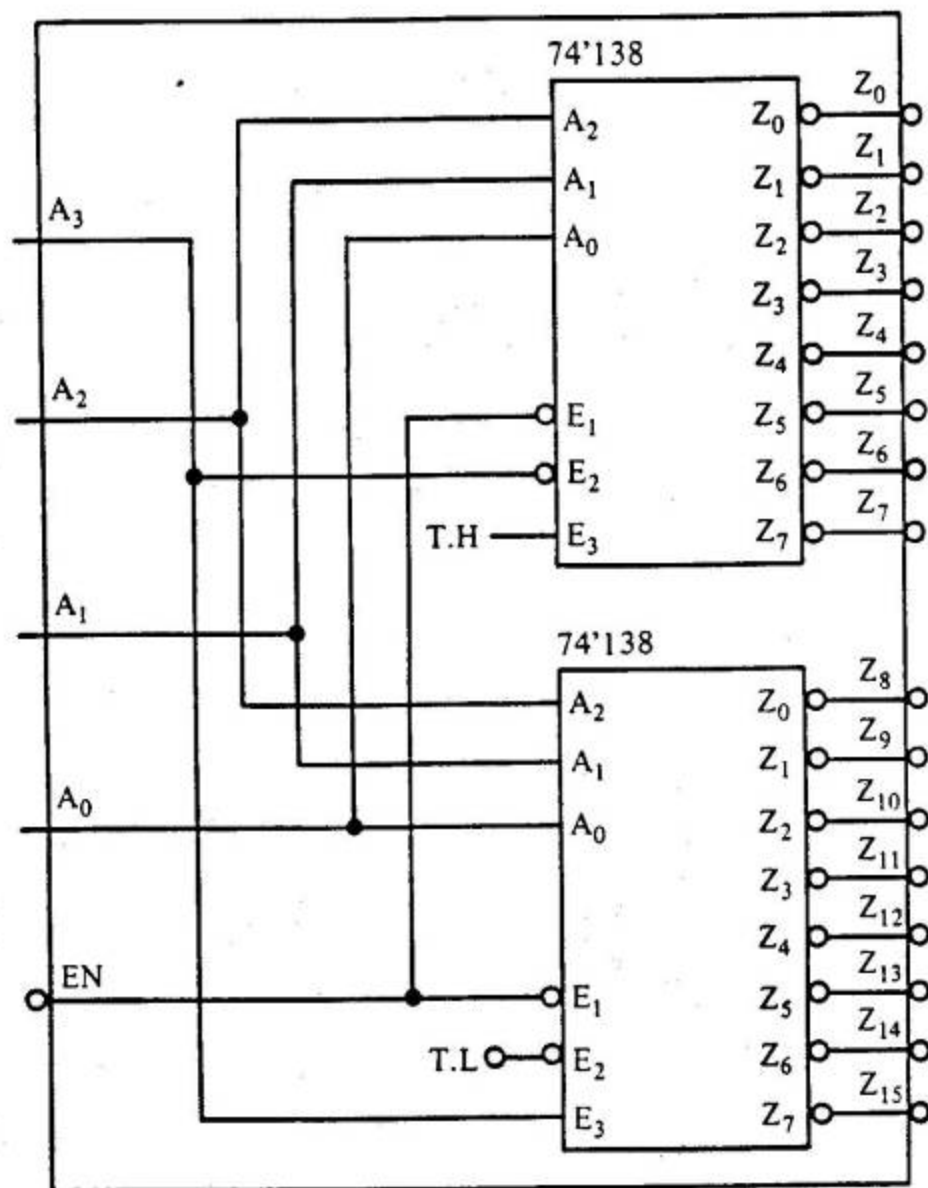


(d) Realization of a 4-to-16 decoder

Figure 4.10 (cont.)

 

(a) A 7-segment display

 

(b) Functional block diagram

D	C	B	A	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	X	X	X	X	X	X	X
1	0	1	1	X	X	X	X	X	X	X
1	1	0	0	X	X	X	X	X	X	X
1	1	0	1	X	X	X	X	X	X	X
1	1	1	0	X	X	X	X	X	X	X
1	1	1	1	X	X	X	X	X	X	X


(c) Truth table

Figure 4.11 BCD-to-7-segment decoder.



74'47

Figure 4.12 74'47 and 74'48 BCD-to-7-segment decoders.

74'48

 

  (a) Functional block diagrams for the 74'47 and 74'48




	Inputs						Outputs							
Decimal or function	LT	RBI	D	C	B	A	BI/RBO	a	b	c	d	e	f	g
0	H	H	L	L	L	L	H	L	L	L	L	L	L	H
1	H	X	L	L	L	H	H	H	L	L	H	H	H	H
2	H	X	L	L	H	L	H	L	L	H	L	L	H	L
3	H	X	L	L	H	H	H	L	L	L	L	H	H	L
4	H	X	L	H	L	L	H	H	L	L	H	H	L	L
5	H	X	L	H	L	H	H	L	H	L	L	H	L	L
6	H	X	L	H	H	L	H	H	H	L	L	L	L	L
7	H	X	L	H	H	H	H	L	L	L	H	H	H	H
8	H	X	H	L	L	L	H	L	L	L	L	L	L	L
9	H	X	H	L	L	H	H	L	L	L	H	H	L	L
10	H	X	H	L	H	L	H	H	H	H	L	L	H	L
11	H	X	H	L	H	H	H	H	H	L	L	H	H	L
12	H	X	H	H	L	L	H	H	L	H	H	H	L	L
13	H	X	H	H	L	H	H	L	H	H	L	H	L	L
14	H	X	H	H	H	L	H	H	H	H	L	L	L	L
15	H	X	H	H	H	H	H	H	H	H	H	H	H	H
BI	X	X	X	X	X	X	L	H	H	H	H	H	H	H
RBI	H	L	L	L	L	L	L	H	H	H	H	H	H	H
LT	L	X	X	X	X	X	H	L	L	L	L	L	L	L

74'47

	Inputs						Outputs							
Decimal or function	LT	RBI	D	C	B	A	BI/RBO	a	b	c	d	e	f	g
0	H	H	L	L	L	L	H	H	H	H	H	H	H	L
1	H	X	L	L	L	H	H	L	H	H	L	L	L	L
2	H	X	L	L	H	L	H	H	H	L	H	H	L	H
3	H	X	L	L	H	H	H	H	H	H	H	L	L	H
4	H	X	L	H	L	L	H	L	H	H	L	L	H	H
5	H	X	L	H	L	H	H	H	L	H	H	L	H	H
6	H	X	L	H	H	L	H	L	L	H	H	H	H	H
7	H	X	L	H	H	H	H	H	H	H	L	L	L	L
8	H	X	H	L	L	L	H	H	H	H	H	H	H	H
9	H	X	H	L	L	H	H	H	H	H	L	L	H	H
10	H	X	H	L	H	L	H	L	L	L	H	H	L	H
11	H	X	H	L	H	H	H	L	L	H	H	L	L	H
12	H	X	H	H	L	L	H	L	H	L	L	L	H	H
13	H	X	H	H	L	H	H	H	L	L	H	L	H	H
14	H	X	H	H	H	L	H	L	L	L	H	H	H	H
15	H	X	H	H	H	H	H	L	L	L	L	L	L	L
BI	X	X	X	X	X	X	L	L	L	L	L	L	L	L
RBI	H	L	L	L	L	L	L	L	L	L	L	L	L	L
LT	L	X	X	X	X	X	H	H	H	H	H	H	H	H


74'48

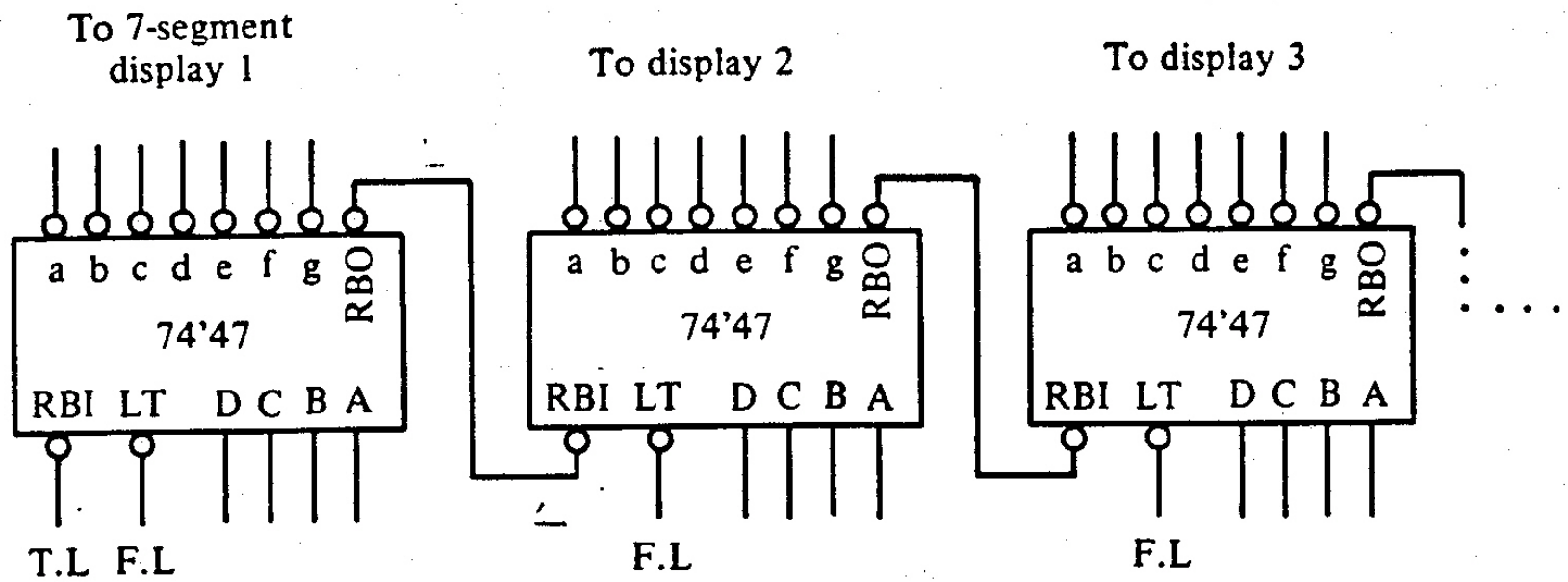(b) Displays and voltage tables for the 74'47 and 74'48



(c) Use of RBI and RBO in a cascade of 7-segment displays

Figure 4.12 74'47 and 74'48 BCD-to-7-segment decoders.

 


(a) Functional block diagram

Figure 4.13 8-to-3 encoder.

I_0	I_1	I_2	I_3	I_4	I_5	I_6	I_7	C_2	C_1	C_0
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

(b) Truth table

 

(a) Functional block diagram

Inputs										Outputs				
EI	0	1	2	3	4	5	6	7		A ₂	A ₁	A ₀	GS	EO
H	X	X	X	X	X	X	X	X		H	H	H	H	H
L	H	H	H	H	H	H	H	H		H	H	H	H	L
L	X	X	X	X	X	X	X	L		L	L	L	L	H
L	X	X	X	X	X	X	L	H		L	L	H	L	H
L	X	X	X	X	X	L	H	H		L	H	L	L	H
L	X	X	X	L	H	H	H	H		H	L	L	L	H
L	X	X	L	H	H	H	H	H		H	L	H	L	H
L	X	L	H	H	H	H	H	H		H	H	L	L	H
L	L	H	H	H	H	H	H	H		H	H	H	L	H

(b) Voltage table

Inputs									Outputs				
EI	0	1	2	3	4	5	6	7	A ₂	A ₁	A ₀	GS	EO
0	X	X	X	X	X	X	X	X	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	0	0	1
1	X	X	X	X	X	X	X	1	1	1	1	1	0
1	X	X	X	X	X	X	1	0	1	1	0	1	0
1	X	X	X	X	X	1	0	0	1	0	1	1	0
1	X	X	X	X	1	0	0	0	1	0	0	1	0
1	X	X	X	1	0	0	0	0	0	1	1	1	0
1	X	X	1	0	0	0	0	0	0	1	0	1	0
1	X	1	0	0	0	0	0	0	0	0	1	1	0
1	1	0	0	0	0	0	0	0	0	0	0	1	0

(c) Truth table

Figure 4.14 74'148 priority encoder.


 



Figure 4.15 *N*-input switch.

 

(a) Functional block diagram


S_1	S_0	Z
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

(b) Condensed truth table

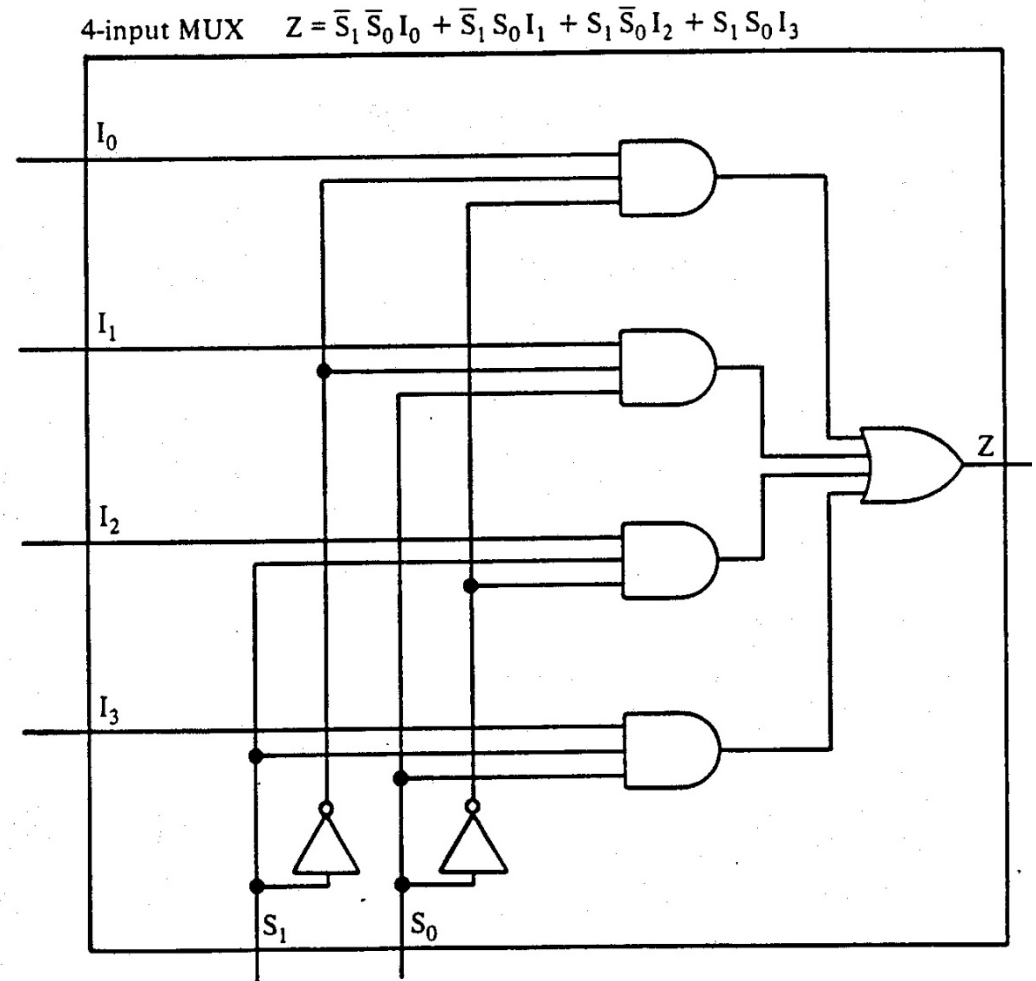

(c) Design and realization

Figure 4.16 Four-input multiplexer.

 

(a) Functional block diagram


E	S ₂	S ₁	S ₀	I ₀	I ₁	I ₂	I ₃	I ₄	I ₅	I ₆	I ₇	\bar{Z}	Z
H	X	X	X	X	X	X	X	X	X	X	X	H	L
L	L	L	L	L	X	X	X	X	X	X	X	H	L
L	L	L	L	H	X	X	X	X	X	X	X	L	H
L	L	L	H	X	L	X	X	X	X	X	X	H	L
L	L	L	H	X	H	X	X	X	X	X	X	L	H
L	L	H	L	X	X	L	X	X	X	X	X	H	L
L	L	H	L	X	X	H	X	X	X	X	X	L	H
L	L	H	H	X	X	X	L	X	X	X	X	H	L
L	L	H	H	X	X	X	H	X	X	X	X	L	H
L	H	L	L	X	X	X	X	L	X	X	X	H	L
L	H	L	L	X	X	X	X	H	X	X	X	L	H
L	H	L	H	X	X	X	X	X	L	X	X	H	L
L	H	L	H	X	X	X	X	X	H	X	X	L	H
L	H	H	L	X	X	X	X	X	X	L	X	H	L
L	H	H	L	X	X	X	X	X	X	H	X	L	H
L	H	H	H	X	X	X	X	X	X	X	L	H	L
L	H	H	H	X	X	X	X	X	X	X	H	L	H

(b) Voltage table


$$Z = E(\bar{S}_2 \bar{S}_1 \bar{S}_0 I_0 + \bar{S}_2 \bar{S}_1 S_0 I_1 + \bar{S}_2 S_1 \bar{S}_0 I_2 + \bar{S}_2 S_1 S_0 I_3 + S_2 \bar{S}_1 \bar{S}_0 I_4 + S_2 \bar{S}_1 S_0 I_5 + S_2 S_1 \bar{S}_0 I_6 + S_2 S_1 S_0 I_7)$$

(c) Logic equation

Figure 4.17 74'151 MUX.

 

(a) N-output switch

 


(b) Functional block diagram

D	S ₁	S ₀	Z ₀	Z ₁	Z ₂	Z ₃
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

(c) Truth table

Figure 4.21 Demultiplexer.

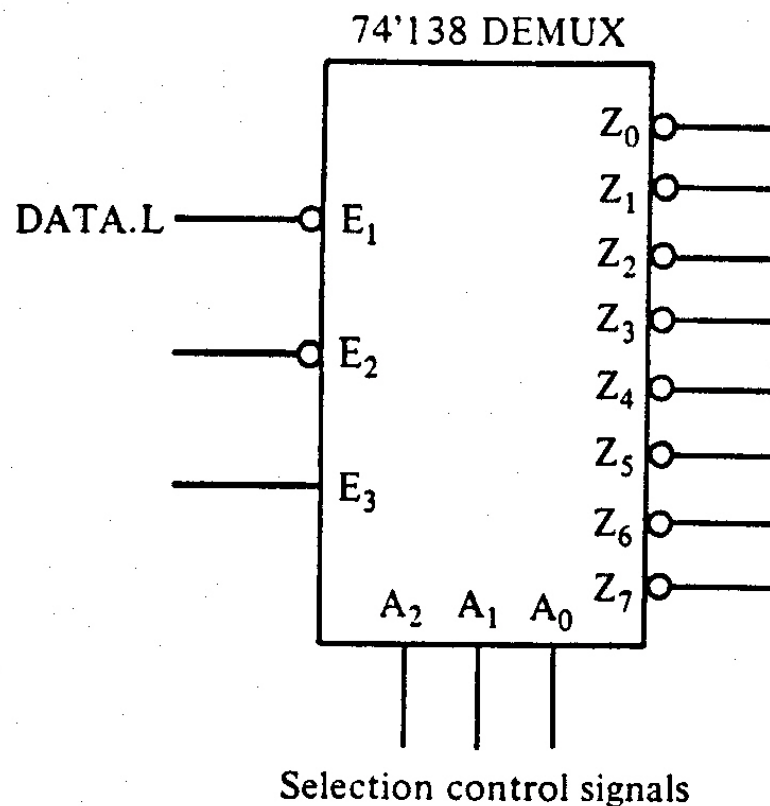

(a) Functional block diagram

Inputs						Outputs							
E ₁	E ₂	E ₃	A ₂	A ₁	A ₀	Z ₀	Z ₁	Z ₂	Z ₃	Z ₄	Z ₅	Z ₆	Z ₇
H	X	X	X	X	X	H	H	H	H	H	H	H	H
X	H	X	X	X	X	H	H	H	H	H	H	H	H
X	X	L	X	X	X	H	H	H	H	H	H	H	H
L	L	H	L	L	L	L	H	H	H	H	H	H	H
L	L	H	L	L	H	H	L	H	H	H	H	H	H
L	L	H	L	H	L	H	H	L	H	H	H	H	H
L	L	H	L	H	H	H	H	H	L	H	H	H	H
L	L	H	H	L	L	H	H	H	H	L	H	H	H
L	L	H	H	L	H	H	H	H	H	H	L	H	H
L	L	H	H	H	L	H	H	H	H	H	H	L	H
L	L	H	H	H	H	H	H	H	H	H	H	H	L

(b) Voltage table

Enable		Data	Selection			Outputs							
E ₂	E ₃	E ₁	A ₂	A ₁	A ₀	Z ₀	Z ₁	Z ₂	Z ₃	Z ₄	Z ₅	Z ₆	Z ₇
X	X	0	X	X	X	0	0	0	0	0	0	0	0
0	X	X	X	X	X	0	0	0	0	0	0	0	0
X	0	X	X	X	X	0	0	0	0	0	0	0	0
1	1	1	0	0	0	1	0	0	0	0	0	0	0
1	1	1	0	0	1	0	1	0	0	0	0	0	0
1	1	1	0	1	0	0	0	1	0	0	0	0	0
1	1	1	0	1	1	0	0	0	1	0	0	0	0
1	1	1	1	0	0	0	0	0	0	1	0	0	0
1	1	1	1	0	1	0	0	0	0	0	1	0	0
1	1	1	1	1	0	0	0	0	0	0	0	1	0
1	1	1	1	1	1	0	0	0	0	0	0	0	1

(c) Truth table

Figure 4.22 74'138 DEMUX.


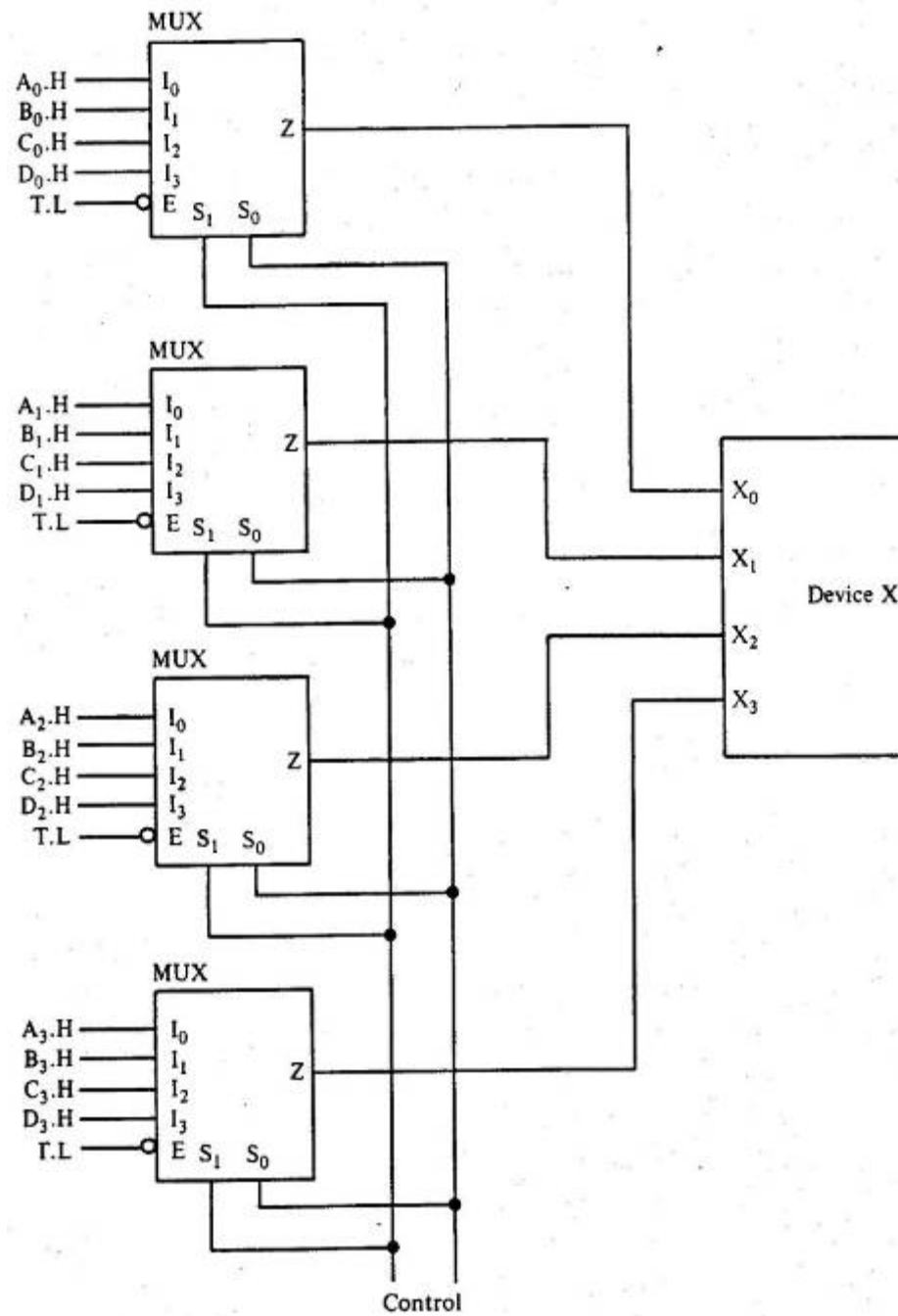


Figure 4.18 Using MUXs for data selection.

 


(a) Functional block diagram

E	D	Y
L	L	L
L	H	H
H	X	(Z)


(Z) = high impedance

(b) Voltage table

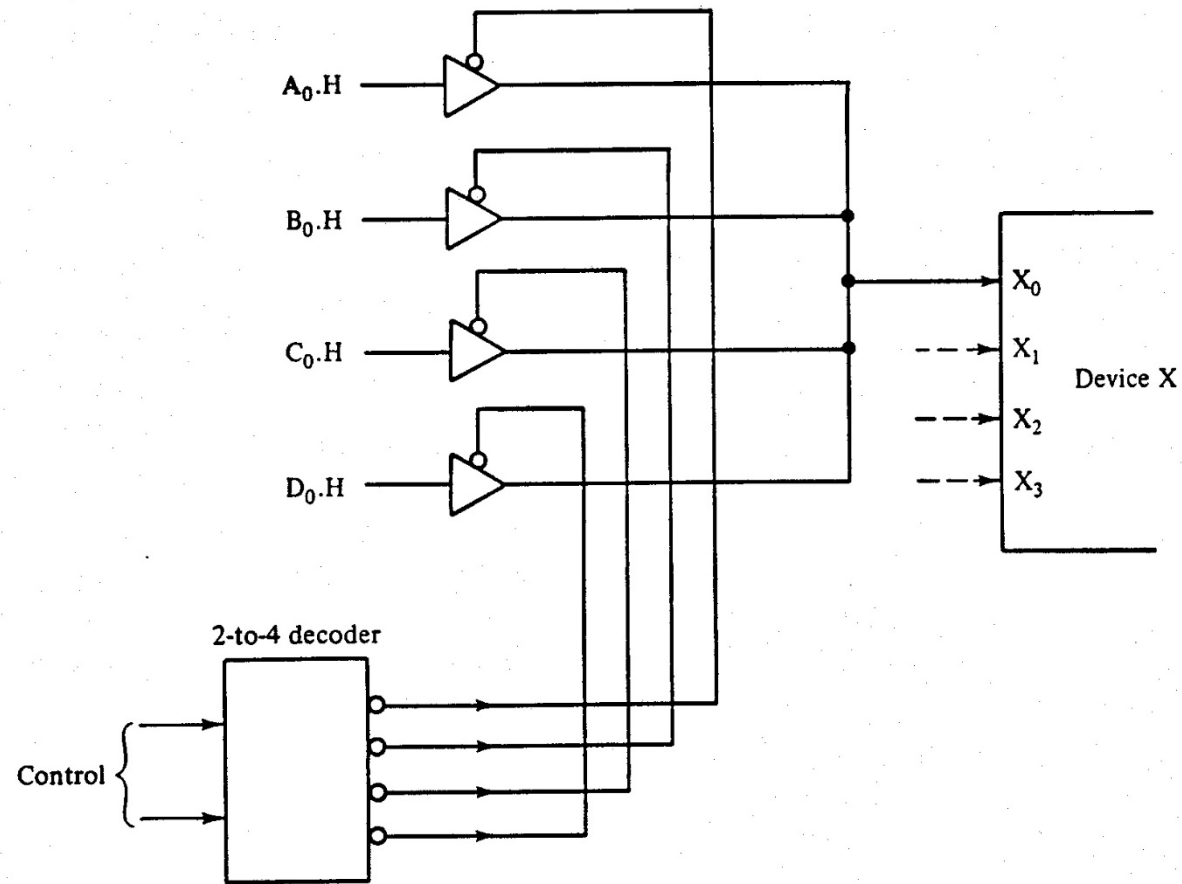

(c) Use of a three-state device for data selection

Figure 4.19 Three-state logic element.

 


(a) Functional block

Select inputs		Data inputs				Output enable	Output
S_1	S_0	I_0	I_1	I_2	I_3	E_0	Z
X	X	X	X	X	X	H	(Z)
L	L	L	X	X	X	L	L
L	L	H	X	X	X	L	H
L	H	X	L	X	X	L	L
L	H	X	H	X	X	L	H
H	L	X	X	L	X	L	L
H	L	X	X	H	X	L	H
H	H	X	X	X	L	L	L
H	H	X	X	X	H	L	H


Where (Z) is a high impedance

(b) Voltage table

Figure 4.20 MUX with three-state outputs.

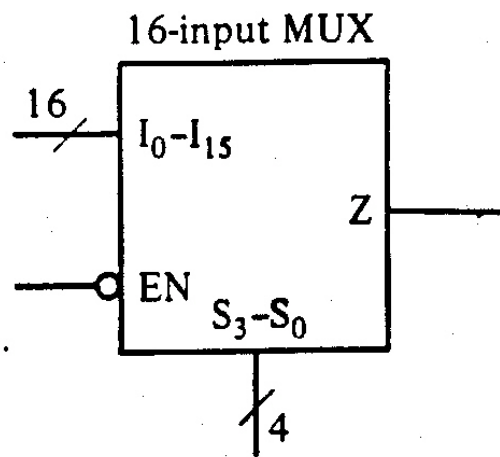


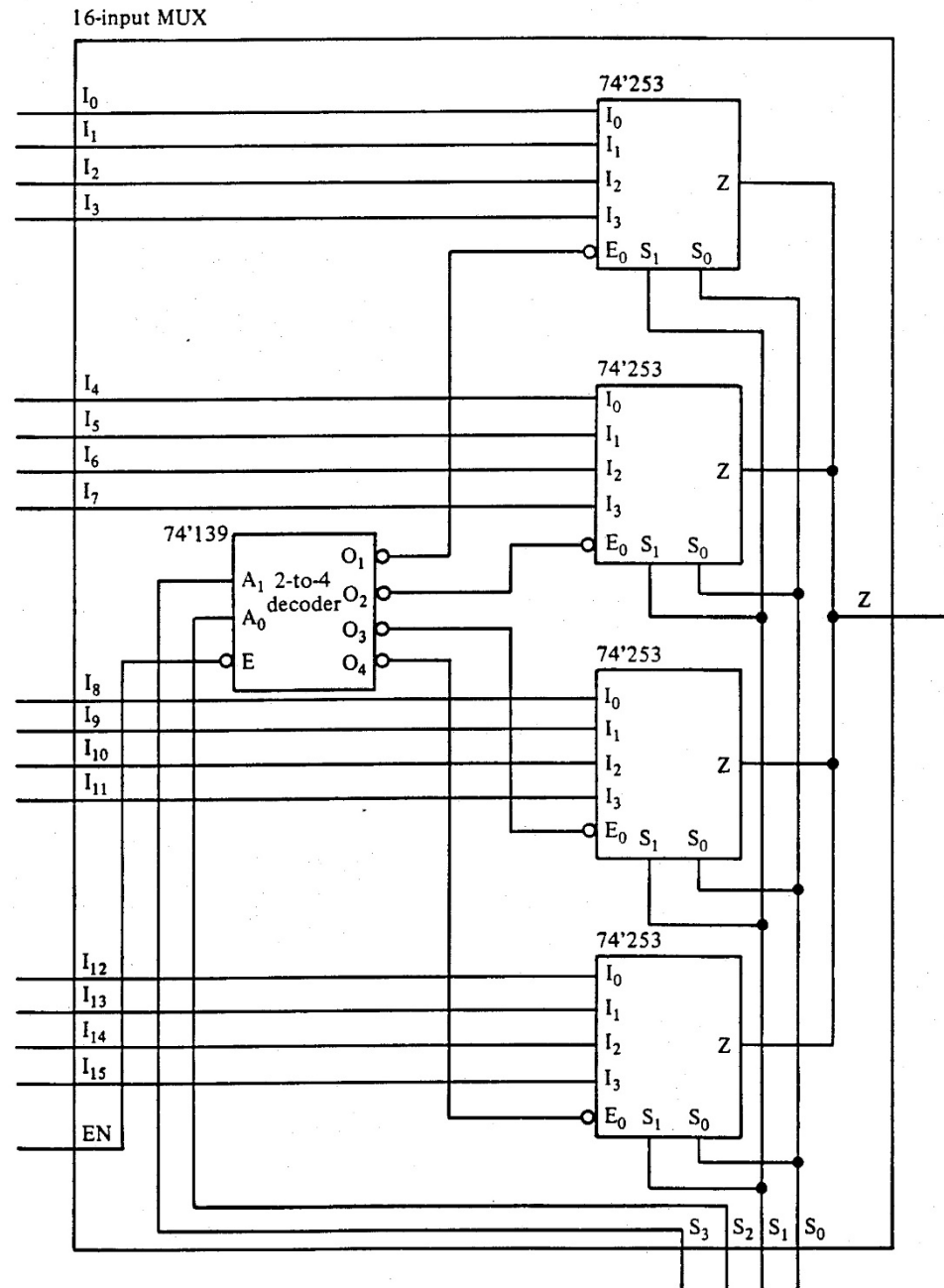(c) Functional block diagram of a 16-input MUX



(d) Realization

Figure 4.20 (cont.)

 

(a) Functional block diagram

A_1	A_0	B_1	B_0	$(A > B)$	$(A = B)$	$(A < B)$
0	0	0	0	0	1	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	1	0	0
0	1	0	1	0	1	0
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	1	0
1	0	1	1	0	0	1
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	0	1	0

(b) Truth table

Figure 4.7 2-bit magnitude comparator.

$\begin{matrix} A_1 & A_0 \\ B_1 & B_0 \end{matrix}$					
		00	01	11	10
00	0	1	1		1
01	0	0	1	1	
11	0	0	0	0	
10	0	0	1		0

$\begin{matrix} A_1 & A_0 \\ B_1 & B_0 \end{matrix}$					
		00	01	11	10
00	1	0	0	0	
01	0	1	0	0	
11	0	0	1	0	
10	0	0	0	1	

$\begin{matrix} A_1 & A_0 \\ B_1 & B_0 \end{matrix}$					
		00	01	11	10
00	0	0	0	0	
01	1	0	0	0	
11	1	1	0	1	
10	1	1	0	0	


$$(A > B) = A_1 \bar{B}_1 + A_0 \bar{B}_1 \bar{B}_0 + A_1 A_0 \bar{B}_0$$

$$(A = B) = \bar{A}_1 \bar{A}_0 \bar{B}_1 \bar{B}_0 + \bar{A}_1 A_0 \bar{B}_1 B_0 + A_1 A_0 B_1 B_0 + A_1 \bar{A}_0 B_1 \bar{B}_0$$

$$(A < B) = \bar{A}_1 B_1 + \bar{A}_1 \bar{A}_0 B_0 + \bar{A}_0 B_1 B_0$$

(c) Design

Figure 4.7 2-bit magnitude comparator.

 


(d) Realization

Figure 4.7 2-bit magnitude comparator.


(a) Functional block diagram

Comparing inputs				Cascading inputs			Outputs		
A_3, B_3	A_2, B_2	A_1, B_1	A_0, B_0	$(A > B).IN$	$(A < B).IN$	$(A = B).IN$	$(A > B)$	$(A < B)$	$(A = B)$
$A_3 > B_3$	X	X	X	X	X	X	H	L	L
$A_3 < B_3$	X	X	X	X	X	X	L	H	L
$A_3 = B_3$	$A_2 > B_2$	X	X	X	X	X	H	L	L
$A_3 = B_3$	$A_2 < B_2$	X	X	X	X	X	L	H	L
$A_3 = B_3$	$A_2 = B_2$	$A_1 > B_1$	X	X	X	X	H	L	L
$A_3 = B_3$	$A_2 = B_2$	$A_1 < B_1$	X	X	X	X	L	H	L
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 > B_0$	X	X	X	H	L	L
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 < B_0$	X	X	X	L	H	L
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$	H	L	L	H	L	L
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$	L	H	L	L	H	L
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$	X	X	H	L	L	H
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$	H	H	L	L	L	L
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$	L	L	L	H	H	L

(b) Voltage table

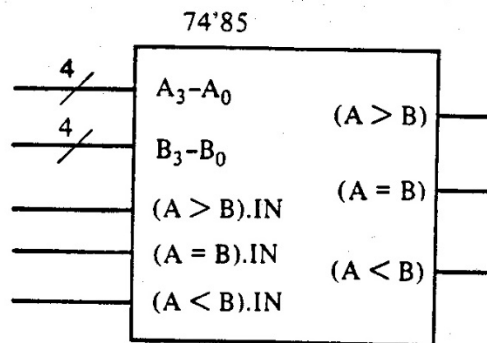

(a) Functional block diagram

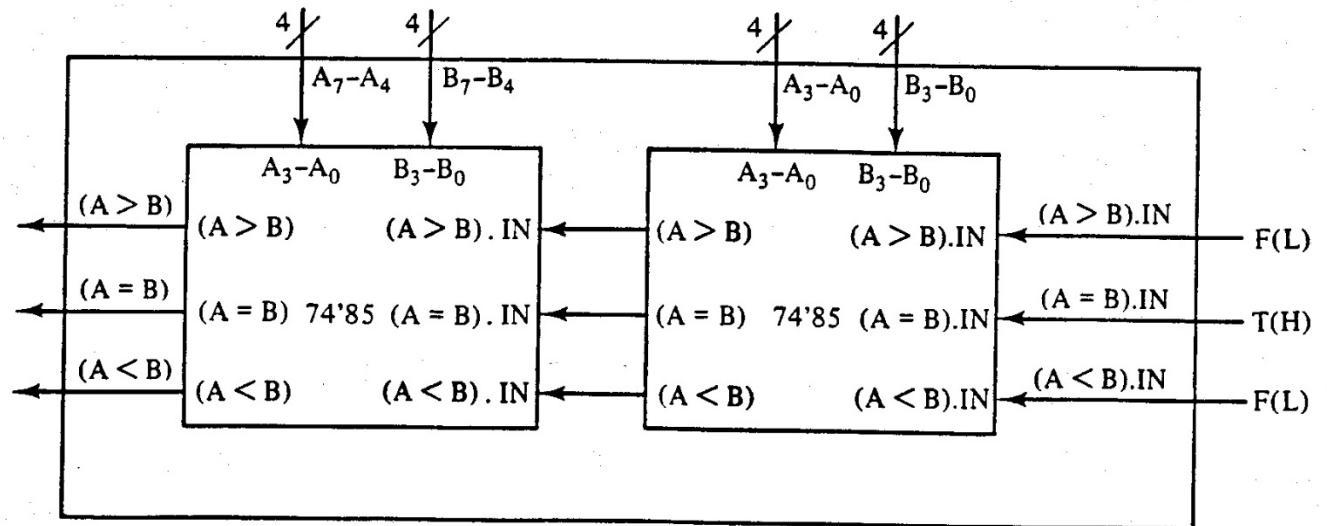

(c) 8-bit magnitude comparator

Figure 4.8 74'85 magnitude comparator.