



EEL3701: Digital Logic & Computer Systems Menu

- Introduction to Logic Design
- Informal Intro to Boolean Algebra
 - > Propositions
 - > Operators
 - > Truth Tables



EEL3701: Digital Logic & Computer Systems Introduction to Logic Design

- Let's logically analyze a simple paragraph:

When I forget my umbrella and it rains, I get wet. I also get wet when I stick my foot in the bathtub when it has already been filled.



EEL3701: Digital Logic & Computer Systems

Logically Analyzing a Paragraph

When I forget my umbrella and it rains, I get wet. I also get wet when I stick my foot in the bathtub when it has already been filled.

OUTPUT:

- The “output” of this paragraph is **“getting wet”**
- I get wet under either of two specified conditions
 - > It rains and I forget my umbrella
 - > The bathtub is filled and I stick my foot in it

University of Florida, EEL 3701 – File 03
© Drs. Schwartz & Arroyo

3



EEL3701: Digital Logic & Computer Systems

Logically Analyzing a Paragraph

When I forget my umbrella and it rains, I get wet. I also get wet when I stick my foot in the bathtub when it has already been filled.

INPUT:

- Each condition is made of of two “inputs”
 - > It rains and I forget my umbrella
 - It rains
 - Forget umbrella
 - > The bathtub is filled and I stick my foot in it
 - Bathtub filled
 - Put foot in it

University of Florida, EEL 3701 – File 03
© Drs. Schwartz & Arroyo

4



EEL3701: Digital Logic & Computer Systems

Signal Abbreviations

When I forget my umbrella and it rains, I get wet. I also get wet when I stick my foot in the bathtub when it has already been filled.

- Let's abbreviate the inputs and outputs

>Output:

- Wet

>Inputs:

- Rain (it rains)
- NoUm (forget umbrella)
- Fill (bathtub filled)
- FootIn (put foot in it)

University of Florida, EEL 3701 – File 03
© Drs. Schwartz & Arroyo

5



EEL3701: Digital Logic & Computer Systems

Writing an Equation

When I forget my umbrella and it rains, I get wet. I also get wet when I stick my foot in the bathtub when it has already been filled.

- Write an “equation” for the paragraph

$$\text{Wet} = (\text{Rain AND NoUm}) \text{ OR } (\text{Fill AND FootIn})$$

University of Florida, EEL 3701 – File 03
© Drs. Schwartz & Arroyo

6



EEL3701: Digital Logic & Computer Systems

Logical Values


- Every logical variable (e.g., Rain, NoUm, ..., Wet) has two possible values
 - > True
 - > False
- The logical abbreviations are:
 - > True: T or 1
 - > False: F or 0




EEL3701: Digital Logic & Computer Systems

Logical **AND** Function

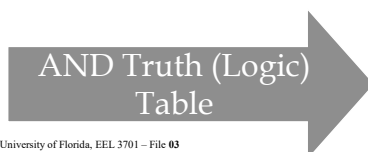- The symbol for a logical AND operation is often one of the symbols used for multiplication: \times , $*$, \bullet , \wedge , or no symbol
 - > $Z = A \times B$
 - > $Z = A * B$
 - > $Z = A \bullet B$
 - > $Z = A \wedge B$
 - > $Z = AB$



A	B	Z=AB
F	F	F
F	T	F
T	F	F
T	T	T

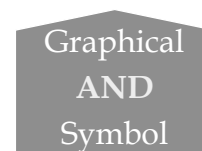



EEL3701: Digital Logic & Computer Systems

Logical **OR** Function

- The symbol for a logical OR operation is often the '+' sign or sometimes 'v',


$$> Z = A + B$$

$$> Z = A \vee B$$

OR Truth (Logic)
Table

A	B	Z=A+B
F	F	F
F	T	T
T	F	T
T	T	T

AND

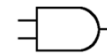

Graphical
OR
Symbol

University of Florida, EEL 3701 – File 03
© Drs. Schwartz & Arroyo

9



EEL3701: Digital Logic & Computer Systems


Logic Circuit

- Logic circuit is easily constructed from the logic equation



$$> Y = AB + C$$

$$> \text{Let } X = AB$$

$$> Y = X + C$$

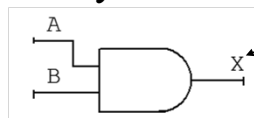

X=AB

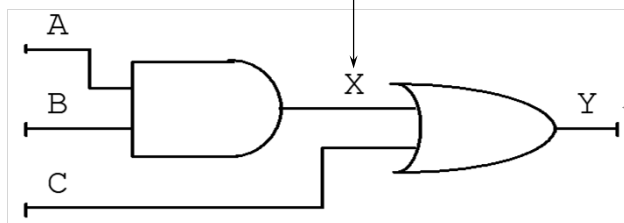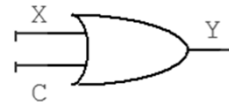

Ready
for Wet?

University of Florida, EEL 3701 – File 03
© Drs. Schwartz & Arroyo


10



EEL3701: Digital Logic & Computer Systems

Design Example: Get Wet!

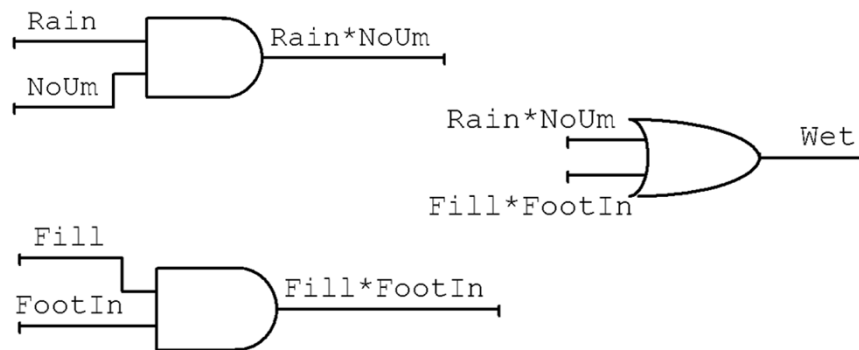- $Wet = (Rain * NoUm) + (Fill * FootIn)$



University of Florida, EEL 3701 – File 03
© Drs. Schwartz & Arroyo


11



EEL3701: Digital Logic & Computer Systems

Design Example: Get Wet!

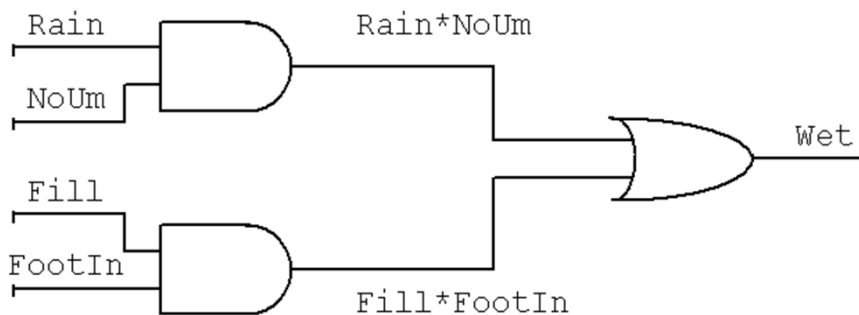- $Wet = (Rain * NoUm) + (Fill * FootIn)$



University of Florida, EEL 3701 – File 03
© Drs. Schwartz & Arroyo

12



EEL3701: Digital Logic & Computer Systems

Logical Level Shift Function


- The symbol for an **INVERTER** operation (also called a **NOT** operator) is one of the following:

$$> Y = /A$$

$$> Y = \overline{A}$$

$$> Y = A'$$


$$> Y = \sim A$$

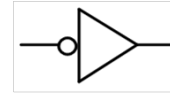

or



A	Y=/A
F	T
T	F

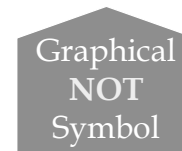University of Florida, EEL 3701 – File 03
© Drs. Schwartz & Arroyo

13



EEL3701: Digital Logic & Computer Systems

Design Example: Stay Dry!


- We can write a whole new paragraph based on the equation **Dry = /Wet**

OLD:

When I forget my umbrella and it rains, I get wet. I also get wet when I stick my foot in the bathtub when it has already been filled.

NEW:

I stay dry if I do not get wet!

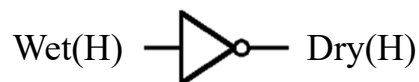University of Florida, EEL 3701 – File 03
© Drs. Schwartz & Arroyo

14



EEL3701: Digital Logic & Computer Systems

Last Logical Example

- What is the equation for the below circuit?

Hint /TwoB

University of Florida, EEL 3701 – File 03
© Drs. Schwartz & Arroyo

15



EEL3701: Digital Logic & Computer Systems

Getting Wet with I/O

- See live simulation with LogicWorks using with inputs and outputs (switches and LEDs)



Get_Wet_action.cct

University of Florida, EEL 3701 – File 03
© Drs. Schwartz & Arroyo

16



EEL3701: Digital Logic & Computer Systems

Intro to Logic Design Summary

- Learned to convert a problem statement into a logic equation
- Learned the basic components of a digital circuit: AND, OR, NOT
- Learned to construct a digital circuit from a logic equation



EEL3701: Digital Logic & Computer Systems

Informal Intro to Boolean Algebra

- Motivation: **Boolean Algebra** is the *calculus of logic*. It is also called *Propositional Logic* or the *calculus of simple assertions*.
- Assertion 1: **Tacos are good.** This is T or F (Not both)
 - > We can express the assertion using symbols, e.g., X, Y, A, B
 - > Let X represent the assertion, then $X=T$ or $X=F$
- Assertion 2: **Tacos are fatty.**
 - > Let Y represent assertion 2, then $Y=T$ or $Y=F$
 - > We can make it more interesting by allowing combinations of assertions and negative sentences (assertions).

Ex: Let $X=T$ and $Y=F$, then

- > “Tacos are **not** good” is false. (We write this as $X' = F$)
- > “Tacos are fatty” is false. ($Y = F$)
- > “Tacos are **not** fatty” is true. ($Y' = F' = T$)

❖X: Tacos are good
❖Y: Tacos are fatty



EEL3701: Digital Logic & Computer Systems

Informal Intro to Boolean Algebra

- Assertion 3: Z: Tacos are cheap. (let $X=T$, $Y=F$, $Z=T$)

Now what does it mean to say:

X and Z (also written as $X * Z$)

T or F ?

❖X: Tacos are good

X or Z (also written as $X + Z$)

T or F ?

❖Y: Tacos are fatty

X and Y (also written as $X * Y$)

T or F ?

❖Z: Tacos are cheap

X or Y (also written as $X + Y$)

T or F ?

The combining of assertions using **AND** is called a **conjunction**, written as XY , $X * Y$, $X \wedge Y$ or $X \bullet Y$, and it is T iff both assertions are T, else it is F.

The combining of assertions using **OR** is called a **disjunction**, written as $X \vee Y$ or $X + Y$, and it is F iff both assertions are F, else it is T.

The combining of assertions using **EOR (XOR)** is called an **exclusive disjunction** (**exclusive or**), written as $X \oplus Y$ or $X :+ Y$, and it is false iff both assertions are either both F or both T, else it is true.

The combining of assertions using **EQUIV** is called an **exclusive conjunction**, (**equivalence**), written as $X \otimes Y$ or $X :: Y$, and it is true iff both assertions are either both F or both are T, else it is false. (This is the complement of the exclusive-OR.)

University of Florida, EEL 3701 – File 03
© Drs. Schwartz & Arroyo

19



EEL3701: Digital Logic & Computer Systems

Activation-Level Notation and Truth Tables

To make the notation easier we assign symbols as follows:

$\{T, F\} = \{1, 0\}$ (= $\{H, L\}$ for positive logic)

or

$\{T, F\} = \{1, 0\}$ (= $\{L, H\}$ for “n” logic)

Since X, Y or Z can only be $\{T, F\}$, we could represent all possibilities exhaustively in a table, called a **Truth Table**

Ex: Represent $X * Y$ and $X + Y$ and $X \oplus Y$ in a Truth Table

X	Y	$X * Y$	$X + Y$	$X \oplus Y$		X	Y	$X * Y$	$X + Y$	$X \oplus Y$
F	F	F	F	F		0	0	0	0	0
F	T	F	T	T		0	1	0	1	1
T	F	F	T	T		1	0	0	1	1
T	T	T	T	F		1	1	1	1	0

University of Florida, EEL 3701 – File 03
© Drs. Schwartz & Arroyo

20



EEL3701: Digital Logic & Computer Systems

History of Boolean Algebra

- Boolean Algebra is so named in honor of **George Boole** who developed the notation in his Ph.D. dissertation in 1847.
 - > **Claude Shannon** applied it to switching networks in 1939.
- Boolean Algebra is the basic mathematics required for the study of the design of digital systems — also called switching networks.
- A switching device is (usually) a two state (binary) device.
 - > We represent the two states of these devices by the symbols $\{0,1\}$ or $\{F,T\}$ or $\{L,H\}$.
 - > It is convenient to use the symbols $\{0,1\}$ as though they were binary numbers, but they are strictly symbols!

University of Florida, EEL 3701 – File 03
© Drs. Schwartz & Arroyo


21



EEL3701: Digital Logic & Computer Systems

Boolean Algebra Notation

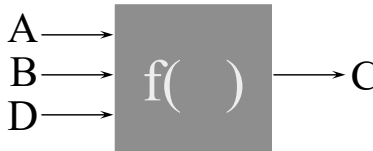- A Boolean variable, usually an uppercase letter, e.g., A, B, X, Y is a variable that can have one and only one state, mainly 0 or 1 (F,T). These variables represent the inputs and outputs of digital devices.
- A Boolean variable may be a function of other Boolean variables, e.g., $C = AB + D \Rightarrow C = f(A,B,D)$.



University of Florida, EEL 3701 – File 03
© Drs. Schwartz & Arroyo

22



EEL3701: Digital Logic & Computer Systems


Inverter, Not, Level Shifter

- The most basic Boolean operations (the basic operations) include: AND, OR, and NOT (complement) .

Definition of NOT:

The complement of a Boolean variable V , written as $\sim V$ (or \overline{V} or $/V$ or V'), is defined as:
 $\sim V = 0$ if $V = 1$ or $\sim V = 1$ if $V = 0$
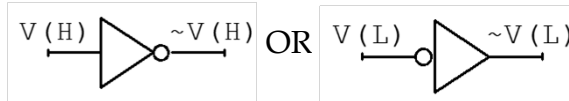
> The electronic device that performs the logical complement operation is called LEVEL SHIFTER (or an INVERTER)



$V(\bullet)$	$\sim V(\bullet)$
F	T
T	F

University of Florida, EEL 3701 – File 03
© Drs. Schwartz & Arroyo

23



EEL3701: Digital Logic & Computer Systems

Informal Intro to Boolean Algebra

- The second most basic Boolean operation is AND.

Definition of AND:

The AND of Boolean variables $\{A, B\}$, written as $A * B$, $A \bullet B$, $A \wedge B$ or AB , is defined as:
 $AB = 1$ iff $A = 1$ and $B = 1$ else $AB = 0$

> The electronic device that performs the logical AND operation is called an AND gate.



A	B	AB
F	F	F
F	T	F
T	F	F
T	T	T

University of Florida, EEL 3701 – File 03
© Drs. Schwartz & Arroyo

24



EEL3701: Digital Logic & Computer Systems

Informal Intro to Boolean Algebra


- The third most basic Boolean operation is OR.

Definition of **OR**:

The OR of Boolean variables $\{A,B\}$, written as $A+B$ or $A \vee B$, is defined as:

$A+B=0$ iff $A=0$ and $B=0$ else $A+B=1$

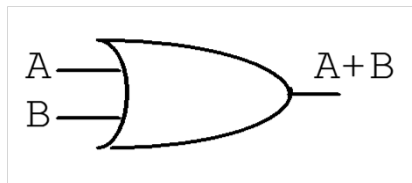- > The electronic device that performs the logical OR operation is called an OR gate.



A	B	A+B
F	F	F
F	T	T
T	F	T
T	T	T

University of Florida, EEL 3701 – File 03
© Drs. Schwartz & Arroyo

25



EEL3701: Digital Logic & Computer Systems

The Mathematics of Logic Design - Boolean Algebra

- Boolean expressions are formed with the basic operations of AND, OR, and NOT being applied to one or more constants or variables.
 - > Parentheses are added as needed to specify the order in which operations are performed
 - > In the absence of parentheses we use the following hierarchy

Priority	Operation	Comments
First	NOT	Individual Variables
Second	AND	
Third	OR	
Last	NOT	On entire expressions

University of Florida, EEL 3701 – File 03
© Drs. Schwartz & Arroyo

26



EEL3701: Digital Logic & Computer Systems

The Mathematics of Logic Design - Boolean Algebra

Definitions:

- **TERMS**: The objects of the universe of discourse, e.g., the constants $[0,1]$, variables, and functions.
- **LITERAL**: A variable or its complement
 >Ex: Let $Z = ABC + AB' + A'BC' + B'C'$. Then this equation has 4 variables (A, B, C, Z) and 11 literals.
- **EQUIVALENCE**: Two Boolean expressions are equivalent iff they have the same values for every possible combination of the variables. Since a Truth Table is an exhaustive (complete) tabulation of the input variables, identical columns imply equivalent (equal) expressions.
- **OBSERVATION**: Each literal in a Boolean expression corresponds to a logic gate input/output.

University of Florida, EEL 3701 – File 03
 © Drs. Schwartz & Arroyo

27



EEL3701: Digital Logic & Computer Systems

The End!

University of Florida, EEL 3701 – File 03
 © Drs. Schwartz & Arroyo

28